

Datapath and Control Unit Implementation

1 Overview

- Each unique component of the datapath and the control unit was designed using Verilog.
- The control unit and datapath components were thoroughly simulated.
- For each component, annotated simulation results are provided.
- All Verilog component code can be seen in Appendix A.
- All test-bench code can be seen in Appendix B.

2 Components

In the sections below, each component of the datapath is described and the its simulation results are discussed.


2.1 Register File

The register file is a multi-port memory array that contains the values of all the registers. The register file accepts three 4-bit inputs, which denote the two registers to be read (R1 and R2) and the register to be written to (RD). It also has a 1-bit write enable (RegW) that controls when a register is written to. The register file also has a 16-bit write data input (WriteData), which contains the value to be written to a register if needed. The register then outputs two 16-bit values (RO1 and RO2), which are the contents of the two registers selected to read.

Inputs: R1 (4-bits), R2 (4-bits), RD (4-bits), RegW (1-bit), WriteData (16-bits)

Outputs: RO1 (16-bits), RO2 (16-bits)

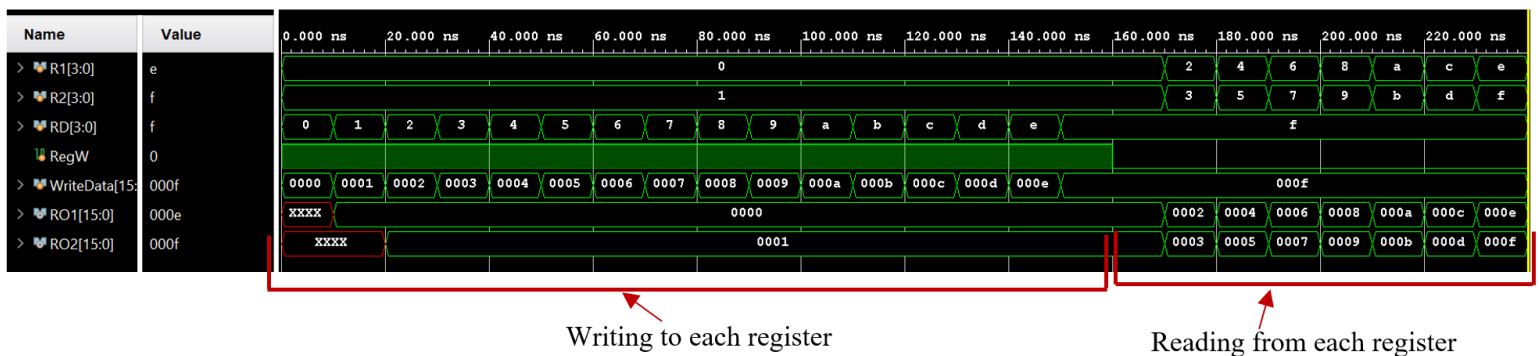In the simulation, a value was written to each register, then each register was read. The simulation results did match the expected output. The simulation waveform and console output can be seen below.



```

R1:  0, R2:  1, RD:  0, RegW: 1, WriteData:  0, RO1:  x, RO2:  x
R1:  0, R2:  1, RD:  1, RegW: 1, WriteData:  1, RO1:  0, RO2:  x
R1:  0, R2:  1, RD:  2, RegW: 1, WriteData:  2, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  3, RegW: 1, WriteData:  3, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  4, RegW: 1, WriteData:  4, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  5, RegW: 1, WriteData:  5, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  6, RegW: 1, WriteData:  6, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  7, RegW: 1, WriteData:  7, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  8, RegW: 1, WriteData:  8, RO1:  0, RO2:  1
R1:  0, R2:  1, RD:  9, RegW: 1, WriteData:  9, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 10, RegW: 1, WriteData: 10, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 11, RegW: 1, WriteData: 11, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 12, RegW: 1, WriteData: 12, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 13, RegW: 1, WriteData: 13, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 14, RegW: 1, WriteData: 14, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 15, RegW: 1, WriteData: 15, RO1:  0, RO2:  1
R1:  0, R2:  1, RD: 15, RegW: 0, WriteData: 15, RO1:  0, RO2:  1
R1:  2, R2:  3, RD: 15, RegW: 0, WriteData: 15, RO1:  2, RO2:  3
R1:  4, R2:  5, RD: 15, RegW: 0, WriteData: 15, RO1:  4, RO2:  5
R1:  6, R2:  7, RD: 15, RegW: 0, WriteData: 15, RO1:  6, RO2:  7
R1:  8, R2:  9, RD: 15, RegW: 0, WriteData: 15, RO1:  8, RO2:  9
R1: 10, R2: 11, RD: 15, RegW: 0, WriteData: 15, RO1: 10, RO2: 11
R1: 12, R2: 13, RD: 15, RegW: 0, WriteData: 15, RO1: 12, RO2: 13
R1: 14, R2: 15, RD: 15, RegW: 0, WriteData: 15, RO1: 14, RO2: 15

```

2.2 ALU

The arithmetic logic unit (ALU) can perform a variety of arithmetic operations. The ALU accepts two 16-bit inputs (A and B), which are the values used in the arithmetic operation. A 4-bit input control signal (ALUOp) indicates what operation is to be performed. The ALU then outputs the 16-bit result (R). It also has three 1-bit output flags: Negative (N), Overflow (O), and Zero (Z).


Inputs: A (16-bits), B (16-bits), ALUOp (4-bits)

Outputs: R (16-bits), O (1-bit), N (1-bit), Z (1-bit)

The ALU operations can be seen in the table below.

ALUOp	Operation
0000	Nothing
0001	Add
0010	AND
0011	NAND
0100	OR
0101	Subtract
0110	Logical Left Shift
0111	Arithmetic Left Shift
1000	Logical Right Shift
1001	Arithmetic Right Shift

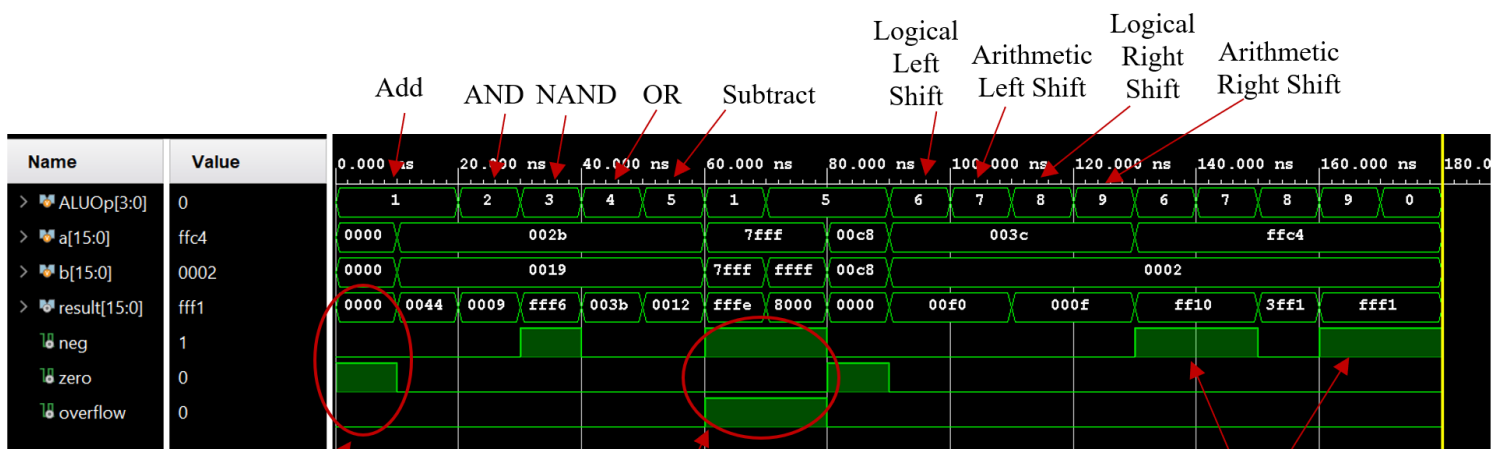In the simulation, each ALU operation was tested. Each operation result was as expected. The flag functionality was also tested. The negative, zero, and overflow flags did function correctly. The simulation waveform and console output can be seen below.



Valid Zero
Flag Set

Neg and Overflow Flag Set
Valid overflow since:
We add two positives and get a negative.
Then, we subtract a negative from a positive and get a negative result.

Valid Neg
Flag Set

```

ALUOp: 1, Input A: 0, Input B: 0, Result: 0, Negative: 0, Zero: 1, Overflow: 0
ALUOp: 1, Input A: 43, Input B: 25, Result: 68, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 2, Input A: 43, Input B: 25, Result: 9, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 3, Input A: 43, Input B: 25, Result: 65526, Negative: 1, Zero: 0, Overflow: 0
ALUOp: 4, Input A: 43, Input B: 25, Result: 59, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 5, Input A: 43, Input B: 25, Result: 18, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 1, Input A: 32767, Input B: 32767, Result: 65534, Negative: 1, Zero: 0, Overflow: 1
ALUOp: 5, Input A: 32767, Input B: 65535, Result: 32768, Negative: 1, Zero: 0, Overflow: 1
ALUOp: 5, Input A: 200, Input B: 200, Result: 0, Negative: 0, Zero: 1, Overflow: 0
ALUOp: 6, Input A: 60, Input B: 2, Result: 240, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 7, Input A: 60, Input B: 2, Result: 240, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 8, Input A: 60, Input B: 2, Result: 15, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 9, Input A: 60, Input B: 2, Result: 15, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 6, Input A: 65476, Input B: 2, Result: 65296, Negative: 1, Zero: 0, Overflow: 0
ALUOp: 7, Input A: 65476, Input B: 2, Result: 65296, Negative: 1, Zero: 0, Overflow: 0
ALUOp: 8, Input A: 65476, Input B: 2, Result: 16369, Negative: 0, Zero: 0, Overflow: 0
ALUOp: 9, Input A: 65476, Input B: 2, Result: 65521, Negative: 1, Zero: 0, Overflow: 0
ALUOp: 0, Input A: 65476, Input B: 2, Result: 65521, Negative: 1, Zero: 0, Overflow: 0

```


2.3 Sign Extender

The sign extender unit extends the sign bit of the input value. The sign extender can accept inputs of varying lengths: In0 (10-bits), In1 (4-bits), In2 (6-bits), and In3 (8-bits). It also has a 2-bit input select signal (SignOp), which determine which input should be extended. The extended value is then outputted as a 16-bit value (ExOut).

Inputs: In0 (10-bits), In1 (4-bits), In2 (6-bits), In3 (8-bits), SignOp (2-bits)

Outputs: ExOut (16-bits)

 In the simulation, various positive and negative numbers were tested. All of the possible input sizes were tested using both positive and negative numbers. The sign extender was observed to function as expected. The simulation waveform and console output can be seen below.



```

SignOp: 0, In0: 186, In1: 6, In2: 13, In3: 37, ExOut: 186
SignOp: 1, In0: 186, In1: 6, In2: 13, In3: 37, ExOut: 6
SignOp: 2, In0: 186, In1: 6, In2: 13, In3: 37, ExOut: 13
SignOp: 3, In0: 186, In1: 6, In2: 13, In3: 37, ExOut: 37
SignOp: 0, In0: 698, In1: 14, In2: 45, In3: 165, ExOut: 65210
SignOp: 1, In0: 698, In1: 14, In2: 45, In3: 165, ExOut: 65534
SignOp: 2, In0: 698, In1: 14, In2: 45, In3: 165, ExOut: 65517
SignOp: 3, In0: 698, In1: 14, In2: 45, In3: 165, ExOut: 65445

```


2.4 Move Extender

The move extender is used for the move lower (movl) and mov upper (movu) instructions. It accepts an 8-bit input (MovIn) and a 1-bit control signal (MovOp). The move extender will place 8 0's to either the bottom or top of the 8-bit input depending on MovOp. The 16-bit value will then be outputted (MovOut).

Inputs: MovIn (8-bits), MovOp (1-bit)

Outputs: MovOut (16-bits)

 In the simulation, various values were tested using both MovOp signals. The move extender was observed to function as expected. The simulation waveform and console output can be seen below.



```

MovOp: 0, MovIn: 255, MovOut: 65280
MovOp: 1, MovIn: 255, MovOut: 255
MovOp: 0, MovIn: 1, MovOut: 256
MovOp: 1, MovIn: 1, MovOut: 1

```


2.5 Adder

There are two adders used in addition to the ALU. Both adders accept two 16-bits inputs (A and B) and output a 16-bit value (Result).

Inputs: A (16-bits), B (16-bits)

Outputs: Result (16-bits)

 In the simulation, various input values were used. The adder did produce the correct result for each of the different input values. The simulation waveform and console output can be seen below.



```

Input A:    0, Input B:    0, Result:    0
Input A:   10, Input B:   20, Result:   30
Input A: 13000, Input B: 20000, Result: 33000
Input A: 16000, Input B:  8000, Result: 24000
Input A: 42000, Input B:    69, Result: 42069

```

2.6 Control Unit

The control unit receives the opcode, LS, R, and AD bits from the instruction memory and sets control signals for the other datapath components in order to execute the proper instruction. The opcode identifies the instruction, LS is used to differentiate load and store, R differentiates jump and return, and AD indicates the direction and arithmetic of shifts. The control unit then outputs: register write enable (RegW), memory read enable (MemR), memory write enable (MemW), branch logic control (BrOp), ALU logic control (ALUOp), move extender control (MovOp), sign extender control (SignOp), and multiplexer control signals (MuxC0 - MuxC4).

Inputs: opcode (4-bits), LS (2-bits), R (1-bit), AD (2-bits)


Outputs: RegW (1-bit), MemR (1-bit), MemW (1-bit), BrOp (3-bits), ALUOp (4-bits), MovOp (1-bit), SignOp (2-bits), MuxC0 (2-bits), MuxC1 (2-bits), MuxC2 (2-bits), MuxC3 (2-bits), MuxC4 (2-bits)

The truth tables for the control unit can be seen below.

Inputs				Outputs						
opcode	R	LS	AD	RegW	MemR	MemW	BrOp	ALUOp	MovOp	SignOp
0001	X	X	X	1	0	0	000	0001	X	X
0010	X	X	X	1	0	0	000	0010	X	X
0011	X	X	X	1	0	0	000	0011	X	X
0100	X	X	X	1	0	0	000	0100	X	X
0101	X	X	X	1	0	0	000	0101	X	X
0110	X	X	X	1	0	0	000	0001	X	11
0111	X	X	X	1	0	0	000	0100	0	X
1000	X	X	X	1	0	0	000	0100	1	X
1001	0	X	X	1	0	0	001	0000	X	00
1001	1	X	X	0	0	0	110	0001	X	X
1010	X	X	X	0	0	0	010	0101	X	01
1011	X	X	X	0	0	0	011	0101	X	01
1100	X	X	X	0	0	0	100	0101	X	01
1101	X	X	X	0	0	0	101	0101	X	01
1110	X	10	X	1	1	0	000	0001	X	X
1110	X	01	X	0	0	1	000	0001	X	X
1111	X	X	00	1	0	0	000	0110	X	10
1111	X	X	10	1	0	0	000	0111	X	10
1111	X	X	01	1	0	0	000	1000	X	10
1111	X	X	11	1	0	0	000	1001	X	10
0000	X	X	X	X	X	X	X	X	X	X

Inputs				Outputs				
opcode	R	LS	AD	MuxC0	MuxC1	MuxC2	MuxC3	MuxC4
0001	X	X	X	00	01	00	00	00
0010	X	X	X	00	01	00	00	00
0011	X	X	X	00	01	00	00	00
0100	X	X	X	00	01	00	00	00
0101	X	X	X	00	01	00	00	00
0110	X	X	X	01	X	00	01	00
0111	X	X	X	01	X	00	10	00
1000	X	X	X	01	X	00	10	00
1001	0	X	X	X	X	10	X	10
1001	1	X	X	10	00	X	00	X
1010	X	X	X	00	01	X	00	X
1011	X	X	X	00	01	X	00	X
1100	X	X	X	00	01	X	00	X
1101	X	X	X	00	01	X	00	X
1110	X	10	X	00	00	00	00	01
1110	X	01	X	01	00	X	00	X
1111	X	X	00	00	X	01	01	00
1111	X	X	10	00	X	01	01	00
1111	X	X	01	00	X	01	01	00
1111	X	X	11	00	X	01	01	00
0000	X	X	X	X	X	X	X	X

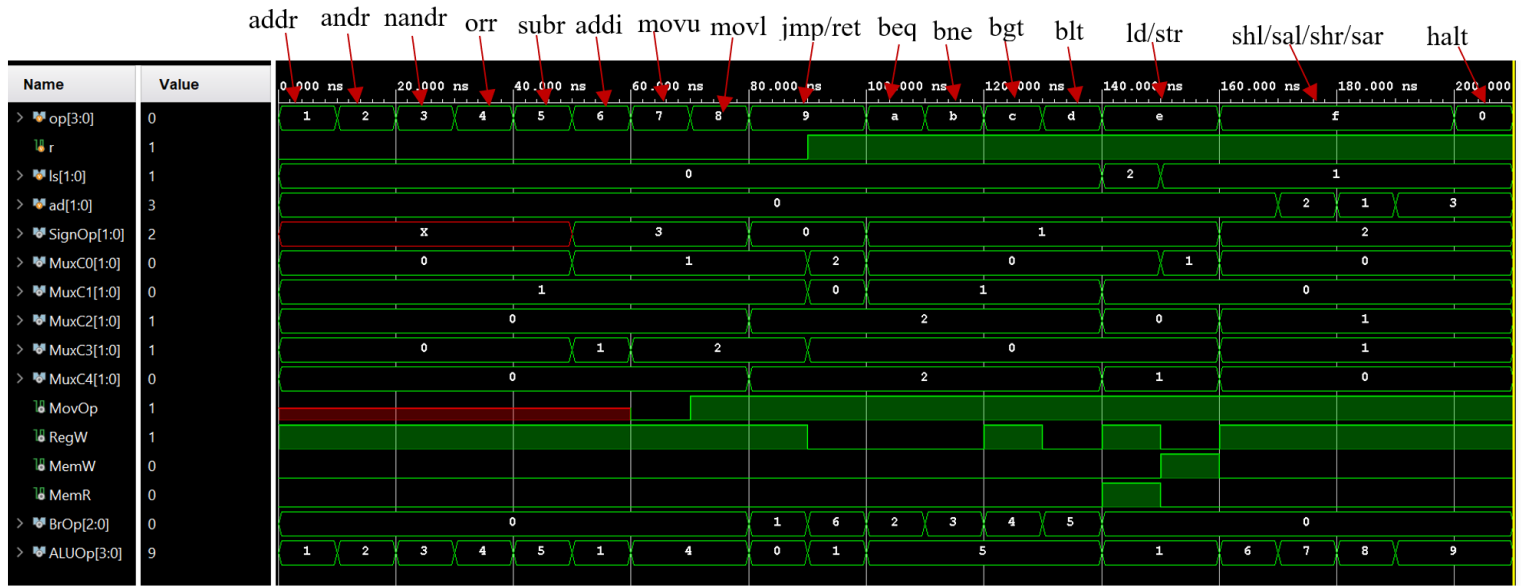In the simulation, each opcode was tested along with the R, LS, and AD fields. The control unit did produce the output described in the above truth tables. The simulation waveform and console output can be seen below.



Inputs

Outputs

Opcode: 1, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 1, MovOp: x, SignOp: x, MuxC0: 0, MuxC1: 1, MuxC2: 0, MuxC3: 0, MuxC4: 0	
Opcode: 2, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 2, MovOp: x, SignOp: x, MuxC0: 0, MuxC1: 1, MuxC2: 0, MuxC3: 0, MuxC4: 0	
Opcode: 3, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 3, MovOp: x, SignOp: x, MuxC0: 0, MuxC1: 1, MuxC2: 0, MuxC3: 0, MuxC4: 0	
Opcode: 4, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 4, MovOp: x, SignOp: x, MuxC0: 0, MuxC1: 1, MuxC2: 0, MuxC3: 0, MuxC4: 0	
Opcode: 5, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 5, MovOp: x, SignOp: x, MuxC0: 0, MuxC1: 1, MuxC2: 0, MuxC3: 0, MuxC4: 0	
Opcode: 6, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 1, MovOp: x, SignOp: 3, MuxC0: 1, MuxC1: 1, MuxC2: 0, MuxC3: 1, MuxC4: 0	
Opcode: 7, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 4, MovOp: 0, SignOp: 3, MuxC0: 1, MuxC1: 1, MuxC2: 0, MuxC3: 2, MuxC4: 0	
Opcode: 8, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 4, MovOp: 1, SignOp: 3, MuxC0: 1, MuxC1: 1, MuxC2: 0, MuxC3: 2, MuxC4: 0	
Opcode: 9, R Field: 0, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 1, ALUOp: 0, MovOp: 1, SignOp: 0, MuxC0: 1, MuxC1: 1, MuxC2: 2, MuxC3: 2, MuxC4: 2	
Opcode: 9, R Field: 1, LS Field: 0, AD Field: 0, RegW: 0, MemR: 0, MemW: 0, BrOp: 6, ALUOp: 1, MovOp: 1, SignOp: 0, MuxC0: 2, MuxC1: 0, MuxC2: 2, MuxC3: 0, MuxC4: 2	
Opcode: 10, R Field: 1, LS Field: 0, AD Field: 0, RegW: 0, MemR: 0, MemW: 0, BrOp: 2, ALUOp: 5, MovOp: 1, SignOp: 1, MuxC0: 0, MuxC1: 1, MuxC2: 2, MuxC3: 0, MuxC4: 2	
Opcode: 11, R Field: 1, LS Field: 0, AD Field: 0, RegW: 0, MemR: 0, MemW: 0, BrOp: 3, ALUOp: 5, MovOp: 1, SignOp: 1, MuxC0: 0, MuxC1: 1, MuxC2: 2, MuxC3: 0, MuxC4: 2	
Opcode: 12, R Field: 1, LS Field: 0, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 4, ALUOp: 5, MovOp: 1, SignOp: 1, MuxC0: 0, MuxC1: 1, MuxC2: 2, MuxC3: 0, MuxC4: 2	
Opcode: 13, R Field: 1, LS Field: 0, AD Field: 0, RegW: 0, MemR: 0, MemW: 0, BrOp: 5, ALUOp: 5, MovOp: 1, SignOp: 1, MuxC0: 0, MuxC1: 1, MuxC2: 2, MuxC3: 0, MuxC4: 2	
Opcode: 14, R Field: 1, LS Field: 2, AD Field: 0, RegW: 1, MemR: 1, MemW: 0, BrOp: 0, ALUOp: 1, MovOp: 1, SignOp: 1, MuxC0: 0, MuxC1: 0, MuxC2: 0, MuxC3: 0, MuxC4: 1	
Opcode: 14, R Field: 1, LS Field: 1, AD Field: 0, RegW: 0, MemR: 0, MemW: 1, BrOp: 0, ALUOp: 1, MovOp: 1, SignOp: 1, MuxC0: 1, MuxC1: 0, MuxC2: 0, MuxC3: 0, MuxC4: 1	
Opcode: 15, R Field: 1, LS Field: 1, AD Field: 0, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 6, MovOp: 1, SignOp: 2, MuxC0: 0, MuxC1: 0, MuxC2: 1, MuxC3: 1, MuxC4: 0	
Opcode: 15, R Field: 1, LS Field: 1, AD Field: 2, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 7, MovOp: 1, SignOp: 2, MuxC0: 0, MuxC1: 0, MuxC2: 1, MuxC3: 1, MuxC4: 0	
Opcode: 15, R Field: 1, LS Field: 1, AD Field: 1, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 8, MovOp: 1, SignOp: 2, MuxC0: 0, MuxC1: 0, MuxC2: 1, MuxC3: 1, MuxC4: 0	
Opcode: 15, R Field: 1, LS Field: 1, AD Field: 3, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 9, MovOp: 1, SignOp: 2, MuxC0: 0, MuxC1: 0, MuxC2: 1, MuxC3: 1, MuxC4: 0	
Opcode: 0, R Field: 1, LS Field: 1, AD Field: 3, RegW: 1, MemR: 0, MemW: 0, BrOp: 0, ALUOp: 9, MovOp: 1, SignOp: 2, MuxC0: 0, MuxC1: 0, MuxC2: 1, MuxC3: 1, MuxC4: 0	

2.7 Branch Control Unit

The branch control unit controls whether a branch or jump is taken. The branch control unit receives a branch logic control (BrOp) signal from the main control unit, which identifies what type of branch or jump is being evaluated. It also accepts the negative (N) and Zero (Z) flags from the ALU to determine whether or not a branch should be taken. The branch control unit then outputs the mux 5 control signal (MuxC5), which determines what value is loaded into the PC.


Inputs: BrOp (3-bits), N (1-bit), Z (1-bit)

Outputs: MuxC5 (2-bits)

The truth table for the branch control unit can be seen below.

Inputs			Outputs
BranchOp	N	Z	MuxC5
000	X	X	00
001	X	X	10
110	X	X	01
010	X	1	10
010	X	0	00
011	X	0	10
011	X	1	00
100	0	0	10
100	1	X	00
101	1	0	10
101	0	X	00

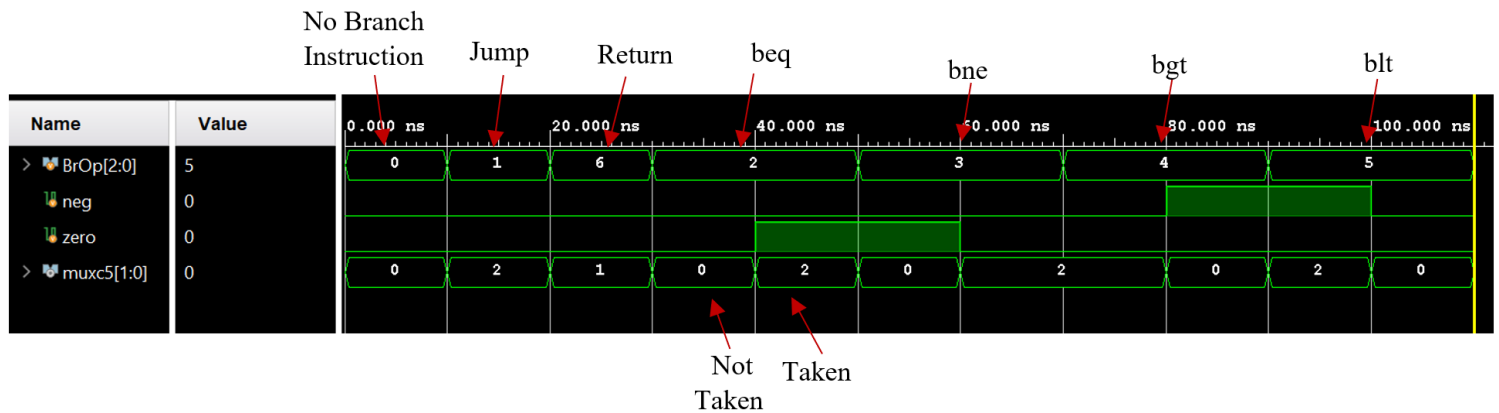In the simulation, each BrOp signal was tested along with various N and Z flags. The branch control unit did produce the output described in the above truth table. The simulation waveform and console output can be seen below.



```

BrOp: 0, Negative: 0, Zero: 0, MuxC5(output): 0
BrOp: 1, Negative: 0, Zero: 0, MuxC5(output): 2
BrOp: 6, Negative: 0, Zero: 0, MuxC5(output): 1
BrOp: 2, Negative: 0, Zero: 0, MuxC5(output): 0
BrOp: 2, Negative: 0, Zero: 1, MuxC5(output): 2
BrOp: 3, Negative: 0, Zero: 1, MuxC5(output): 0
BrOp: 3, Negative: 0, Zero: 0, MuxC5(output): 2
BrOp: 4, Negative: 0, Zero: 0, MuxC5(output): 2
BrOp: 4, Negative: 1, Zero: 0, MuxC5(output): 0
BrOp: 5, Negative: 1, Zero: 0, MuxC5(output): 2
BrOp: 5, Negative: 0, Zero: 0, MuxC5(output): 0


```

2.8 4-to-1 Multiplexer

Several 4-to-1 multiplexers are used throughout the datapath to select one output from multiple inputs. The multiplexers used throughout the datapath are listed below. Each multiplexer has a control signal (MuxC#) from the control unit, which selects what input to pass.

In the simulation, various control signals were used to pass each of the four inputs. The multiplexer was observed to work correctly. The simulation waveform and console

output can be seen below.

 


```
Control: 0, Input A: 1, Input B: 2, Input C: 3, Input D: 4, Output: 1
Control: 1, Input A: 1, Input B: 2, Input C: 3, Input D: 4, Output: 2
Control: 2, Input A: 1, Input B: 2, Input C: 3, Input D: 4, Output: 3
Control: 3, Input A: 1, Input B: 2, Input C: 3, Input D: 4, Output: 4
```

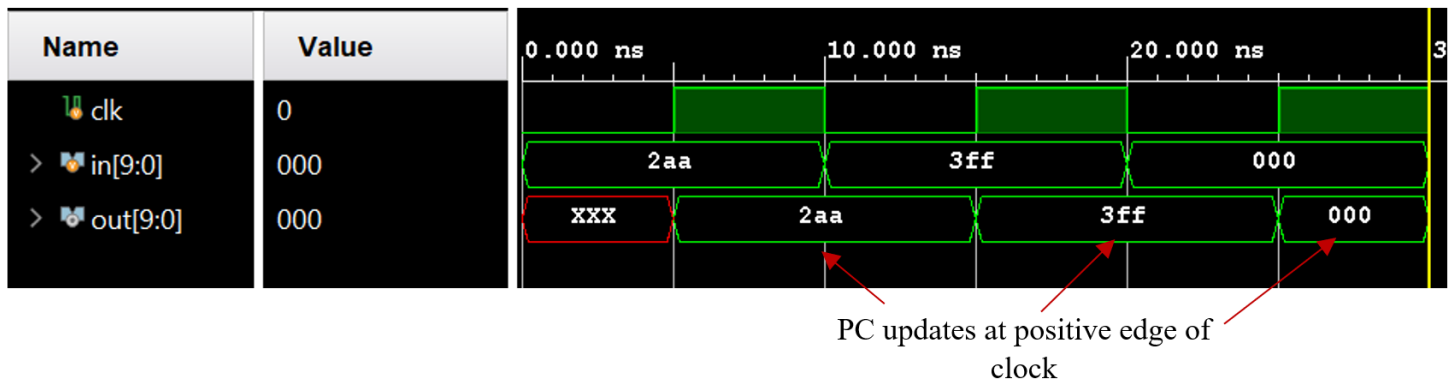2.9 Program Counter

The program counter is a 10-bit register that holds the address of the next instruction. The PC will be updated when the positive edge of the clock is detected. This change will then trigger changes in all the other datapath components in order to execute the desired instruction.

In the simulation, various inputs were used along with a clock signal. The PC was observed to only update when the positive edge of the clock was detected. Thus, the PC performed correctly. The simulation waveform and console output can be seen below.



```

Clock: 0, In:  682, Out:    x
Clock: 1, In:  682, Out:  682
Clock: 0, In: 1023, Out:  682
Clock: 1, In: 1023, Out: 1023
Clock: 0, In:    0, Out: 1023
Clock: 1, In:    0, Out:    0
Clock: 0, In:    0, Out:    0

```

Appendix A Component Code

A.1 Register File

```
1 module reg_file(R1, R2, RD, RegW, WriteData, R01, R02);
2     input [3:0] R1;
3     input [3:0] R2;
4     input [3:0] RD;
5     input RegW;
6     input [15:0] WriteData;
7     output reg [15:0] R01;
8     output reg [15:0] R02;
9     reg [15:0] regs [15:0];
10
11     always @ (R1 or R2 or RD or RegW or WriteData)
12     begin
13         if (RegW == 1)
14             regs[RD] <= WriteData;
15             R01 <= regs[R1];
16             R02 <= regs[R2];
17     end
18 endmodule
```

A.2 ALU

```
1 module alu(ALUOp, a, b, r, n, z, o);
2     input [3:0] ALUOp;
3     input signed [15:0] a;
4     input signed [15:0] b;
5     output reg [15:0] r;
6     output reg n, z, o;
7
8     always @*
9     begin
10         n = 0;
11         z = 0;
12         o = 0;
13         case (ALUOp)
14             4'b0000: r = r;
15             4'b0001: begin
16                 r = a + b; o = (a[15] ^ b[15]) ? 0:(r[15] ^ a[15]);
```



```

17         end
18         4'b0010: r = a & b;
19         4'b0011: r = ~(a & b);
20         4'b0100: r = a | b;
21         4'b0101: begin
22             r = a - b; o = (a[15] ^ b[15]) ? (r[15] ^^ b[15]):0;
23         end
24         4'b0110: r = a << b;
25         4'b0111: r = a <<< b;
26         4'b1000: r = a >> b;
27         4'b1001: r = a >>> b;
28         default: r = 0;
29     endcase
30     n = (r[15] == 1'b1) ? 1:0;
31     z = (r == 0) ? 1:0;
32 end
33 endmodule

```

A.3 Sign Extender

```

1 module sign_ext(SignOp, In0, In1, In2, In3, ExOut);
2     input [1:0] SignOp;
3     input [9:0] In0;
4     input [3:0] In1;
5     input [5:0] In2;
6     input [7:0] In3;
7     output reg [15:0] ExOut;
8
9     always @ (SignOp or In0 or In1 or In2 or In3)
10     begin
11         case (SignOp)
12             2'b00: ExOut = { {6{In0[9]}} , In0 };
13             2'b01: ExOut = { {12{In1[3]}} , In1 };
14             2'b10: ExOut = { {10{In2[5]}} , In2 };
15             2'b11: ExOut = { {8{In3[7]}} , In3 };
16         endcase
17     end
18 endmodule

```

A.4 Move Extender

```
1 module mov_ext(MovOp, MovIn, MovOut);
2     input MovOp;
3     input [7:0] MovIn;
4     output reg [15:0] MovOut;
5
6     always @ (MovOp or MovIn)
7     begin
8         if (MovOp == 0)
9             MovOut = { MovIn, {8{1'b0}} };
10        else if (MovOp == 1)
11            MovOut = { {8{1'b0}}, MovIn };
12    end
13 endmodule
```

A.5 Adder

```
1 module adder(a, b, y);
2     input [15:0] a;
3     input [15:0] b;
4     output reg [15:0] y;
5
6     always @ (a or b)
7     begin
8         y = a + b;
9     end
10 endmodule
```

A.6 Control Unit

```
1 module control(op, r, ls, ad, RegW, MemR, MemW, BrOp, ALUOp, MovOp,
2               SignOp, MuxC0, MuxC1, MuxC2, MuxC3, MuxC4);
3     input [3:0] op;
4     input r;
5     input [1:0] ls, ad;
6     output reg [1:0] SignOp, MuxC0, MuxC1, MuxC2, MuxC3, MuxC4;
7     output reg MovOp, RegW, MemW, MemR;
8     output reg [2:0] BrOp;
9     output reg [3:0] ALUOp;
```

```
10
11     always @ (op or r or ls or ad)
12     begin
13         case(op)
14             4'b0001: begin
15                 RegW <= 1'b1;
16                 MemR <= 1'b0;
17                 MemW <= 1'b0;
18                 BrOp <= 3'b000;
19                 ALUOp <= 4'b0001;
20                 MuxC0 <= 2'b00;
21                 MuxC1 <= 2'b01;
22                 MuxC2 <= 2'b00;
23                 MuxC3 <= 2'b00;
24                 MuxC4 <= 2'b00;
25             end
26             4'b0010: begin
27                 RegW <= 1'b1;
28                 MemR <= 1'b0;
29                 MemW <= 1'b0;
30                 BrOp <= 3'b000;
31                 ALUOp <= 4'b0010;
32                 MuxC0 <= 2'b00;
33                 MuxC1 <= 2'b01;
34                 MuxC2 <= 2'b00;
35                 MuxC3 <= 2'b00;
36                 MuxC4 <= 2'b00;
37             end
38             4'b0011: begin
39                 RegW <= 1'b1;
40                 MemR <= 1'b0;
41                 MemW <= 1'b0;
42                 BrOp <= 3'b000;
43                 ALUOp <= 4'b0011;
44                 MuxC0 <= 2'b00;
45                 MuxC1 <= 2'b01;
46                 MuxC2 <= 2'b00;
47                 MuxC3 <= 2'b00;
48                 MuxC4 <= 2'b00;
49             end
50             4'b0100: begin
51                 RegW <= 1'b1;
```

```
52         MemR <= 1'b0;
53         MemW <= 1'b0;
54         BrOp <= 3'b000;
55         ALUOp <= 4'b0100;
56         MuxC0 <= 2'b00;
57         MuxC1 <= 2'b01;
58         MuxC2 <= 2'b00;
59         MuxC3 <= 2'b00;
60         MuxC4 <= 2'b00;
61     end
62     4'b0101: begin
63         RegW <= 1'b1;
64         MemR <= 1'b0;
65         MemW <= 1'b0;
66         BrOp <= 3'b000;
67         ALUOp <= 4'b0101;
68         MuxC0 <= 2'b00;
69         MuxC1 <= 2'b01;
70         MuxC2 <= 2'b00;
71         MuxC3 <= 2'b00;
72         MuxC4 <= 2'b00;
73     end
74     4'b0110: begin
75         RegW <= 1'b1;
76         MemR <= 1'b0;
77         MemW <= 1'b0;
78         BrOp <= 3'b000;
79         ALUOp <= 4'b0001;
80         SignOp <= 2'b11;
81         MuxC0 <= 2'b01;
82         MuxC2 <= 2'b00;
83         MuxC3 <= 2'b01;
84         MuxC4 <= 2'b00;
85     end
86     4'b0111: begin
87         RegW <= 1'b1;
88         MemR <= 1'b0;
89         MemW <= 1'b0;
90         BrOp <= 3'b000;
91         ALUOp <= 4'b0100;
92         MovOp <= 1'b0;
93         MuxC0 <= 2'b01;
```

```
94         MuxC2 <= 2'b00;
95         MuxC3 <= 2'b10;
96         MuxC4 <= 2'b00;
97     end
98     4'b1000: begin
99         RegW <= 1'b1;
100        MemR <= 1'b0;
101        MemW <= 1'b0;
102        BrOp <= 3'b000;
103        ALUOp <= 4'b0100;
104        MovOp <= 1'b1;
105        MuxC0 <= 2'b01;
106        MuxC2 <= 2'b00;
107        MuxC3 <= 2'b10;
108        MuxC4 <= 2'b00;
109    end
110    4'b1001: begin
111        if (r == 1'b0)
112            begin
113                RegW <= 1'b1;
114                MemR <= 1'b0;
115                MemW <= 1'b0;
116                BrOp <= 3'b001;
117                ALUOp <= 4'b0000;
118                SignOp <= 2'b00;
119                MuxC2 <= 2'b10;
120                MuxC4 <= 2'b10;
121            end
122        else if (r == 1'b1)
123            begin
124                RegW <= 1'b0;
125                MemR <= 1'b0;
126                MemW <= 1'b0;
127                BrOp <= 3'b110;
128                ALUOp <= 4'b0001;
129                MuxC0 <= 2'b10;
130                MuxC1 <= 2'b00;
131                MuxC3 <= 2'b00;
132            end
133        end
134    4'b1010: begin
135        RegW <= 1'b0;
```

```
136         MemR <= 1'b0;
137         MemW <= 1'b0;
138         BrOp <= 3'b010;
139         ALUOp <= 4'b0101;
140         SignOp <= 2'b01;
141         MuxC0 <= 2'b00;
142         MuxC1 <= 2'b01;
143         MuxC3 <= 2'b00;
144     end
145     4'b1011: begin
146         RegW <= 1'b0;
147         MemR <= 1'b0;
148         MemW <= 1'b0;
149         BrOp <= 3'b011;
150         ALUOp <= 4'b0101;
151         SignOp <= 2'b01;
152         MuxC0 <= 2'b00;
153         MuxC1 <= 2'b01;
154         MuxC3 <= 2'b00;
155     end
156     4'b1100: begin
157         RegW <= 1'b1;
158         MemR <= 1'b0;
159         MemW <= 1'b0;
160         BrOp <= 3'b100;
161         ALUOp <= 4'b0101;
162         SignOp <= 2'b01;
163         MuxC0 <= 2'b00;
164         MuxC1 <= 2'b01;
165         MuxC3 <= 2'b00;
166     end
167     4'b1101: begin
168         RegW <= 1'b0;
169         MemR <= 1'b0;
170         MemW <= 1'b0;
171         BrOp <= 3'b101;
172         ALUOp <= 4'b0101;
173         SignOp <= 2'b01;
174         MuxC0 <= 2'b00;
175         MuxC1 <= 2'b01;
176         MuxC3 <= 2'b00;
177     end
```

```
178         4'b1110: begin
179             if (ls == 2'b10)
180                 begin
181                     RegW <= 1'b1;
182                     MemR <= 1'b1;
183                     MemW <= 1'b0;
184                     BrOp <= 3'b000;
185                     ALUOp <= 4'b0001;
186                     MuxC0 <= 2'b00;
187                     MuxC1 <= 2'b00;
188                     MuxC2 <= 2'b00;
189                     MuxC3 <= 2'b00;
190                     MuxC4 <= 2'b01;
191                 end
192             else if (ls == 2'b01)
193                 begin
194                     RegW <= 1'b0;
195                     MemR <= 1'b0;
196                     MemW <= 1'b1;
197                     BrOp <= 3'b000;
198                     ALUOp <= 4'b0001;
199                     MuxC0 <= 2'b01;
200                     MuxC1 <= 2'b00;
201                     MuxC3 <= 2'b00;
202                 end
203             end
204         4'b1111: begin
205             if (ad == 2'b00)
206                 begin
207                     RegW <= 1'b1;
208                     MemR <= 1'b0;
209                     MemW <= 1'b0;
210                     BrOp <= 3'b000;
211                     ALUOp <= 4'b0110;
212                     SignOp <= 2'b10;
213                     MuxC0 <= 2'b00;
214                     MuxC2 <= 2'b01;
215                     MuxC3 <= 2'b01;
216                     MuxC4 <= 2'b00;
217                 end
218             else if (ad == 2'b10)
219                 begin
```

```
220         RegW <= 1'b1;
221         MemR <= 1'b0;
222         MemW <= 1'b0;
223         BrOp <= 3'b000;
224         ALUOp <= 4'b0111;
225         SignOp <= 2'b10;
226         MuxC0 <= 2'b00;
227         MuxC2 <= 2'b01;
228         MuxC3 <= 2'b01;
229         MuxC4 <= 2'b00;
230     end
231     else if (ad == 2'b01)
232     begin
233         RegW <= 1'b1;
234         MemR <= 1'b0;
235         MemW <= 1'b0;
236         BrOp <= 3'b000;
237         ALUOp <= 4'b1000;
238         SignOp <= 2'b10;
239         MuxC0 <= 2'b00;
240         MuxC2 <= 2'b01;
241         MuxC3 <= 2'b01;
242         MuxC4 <= 2'b00;
243     end
244     else if (ad == 2'b11)
245     begin
246         RegW <= 1'b1;
247         MemR <= 1'b0;
248         MemW <= 1'b0;
249         BrOp <= 3'b000;
250         ALUOp <= 4'b1001;
251         SignOp <= 2'b10;
252         MuxC0 <= 2'b00;
253         MuxC2 <= 2'b01;
254         MuxC3 <= 2'b01;
255         MuxC4 <= 2'b00;
256     end
257 end
258 endcase
259 end
260 endmodule
```


A.7 Branch Control Unit

```
1 module branch_control(BrOp, neg, zero, muxc5);
2     input [2:0] BrOp;
3     input neg;
4     input zero;
5     output reg [1:0] muxc5;
6
7     always @ (BrOp, neg, zero)
8     begin
9         case(BrOp)
10            3'b000: muxc5 = 2'b00;
11            3'b001: muxc5 = 2'b10;
12            3'b110: muxc5 = 2'b01;
13            3'b010: muxc5 = (zero == 1'b1) ? 2'b10:2'b00;
14            3'b011: muxc5 = (zero == 1'b1) ? 2'b00:2'b10;
15            3'b100: muxc5 = (neg == 1'b1) ? 2'b00:2'b10;
16            3'b101: muxc5 = (neg == 1'b1) ? 2'b10:2'b00;
17        endcase
18    end
19 endmodule
```

A.8 4-to-1 Multiplexer

```
1 module mux_4to1(control, a, b, c, d, out);
2     input [1:0] control;
3     input [15:0] a;
4     input [15:0] b;
5     input [15:0] c;
6     input [15:0] d;
7     output reg [15:0] out;
8
9     always @ (control or a or b or c or d)
10    begin
11        case (control)
12            2'b00: out = a;
13            2'b01: out = b;
14            2'b10: out = c;
15            2'b11: out = d;
16        endcase
17    end
```

```
18 endmodule
```

A.9 Program Counter

```
1 module pc(clk, in, out);
2     input clk;
3     input [9:0] in;
4     output reg [9:0] out;
5
6     always @ (posedge clk)
7     begin
8         out = in;
9     end
10 endmodule
```

Appendix B Test-bench Code

B.1 Register File

```
1 module reg_file_tb();
2     reg [3:0] R1;
3     reg [3:0] R2;
4     reg [3:0] RD;
5     reg RegW;
6     reg [15:0] WriteData;
7     wire [15:0] R01;
8     wire [15:0] R02;
9
10     reg_file REG (R1, R2, RD, RegW, WriteData, R01, R02);
11
12     initial
13     begin
14         $monitor("R1: %d, R2: %d, RD: %d, RegW: %d, WriteData: %d,
15                 R01: %d, R02: %d", R1, R2, RD, RegW, WriteData, R01, R02);
16         RegW = 1; RD = 0; WriteData = 0; R1 = 0; R2 = 1;
17         #10; RD = 1; WriteData = 1;
18         #10; RD = 2; WriteData = 2;
19         #10; RD = 3; WriteData = 3;
20         #10; RD = 4; WriteData = 4;
```

```
21      #10; RD = 5; WriteData = 5;
22      #10; RD = 6; WriteData = 6;
23      #10; RD = 7; WriteData = 7;
24      #10; RD = 8; WriteData = 8;
25      #10; RD = 9; WriteData = 9;
26      #10; RD = 10; WriteData = 10;
27      #10; RD = 11; WriteData = 11;
28      #10; RD = 12; WriteData = 12;
29      #10; RD = 13; WriteData = 13;
30      #10; RD = 14; WriteData = 14;
31      #10; RD = 15; WriteData = 15;
32      #10; RegW = 0; R1 = 0; R2 = 1;
33      #10; R1 = 2; R2 = 3;
34      #10; R1 = 4; R2 = 5;
35      #10; R1 = 6; R2 = 7;
36      #10; R1 = 8; R2 = 9;
37      #10; R1 = 10; R2 = 11;
38      #10; R1 = 12; R2 = 13;
39      #10; R1 = 14; R2 = 15;
40      end
41  endmodule
```

B.2 ALU

```
1  module alu_tb();
2      reg [3:0] ALUOp;
3      reg [15:0] a;
4      reg [15:0] b;
5      wire [15:0] result;
6      wire neg, zero, overflow;
7
8      alu ALU1 (ALUOp, a, b, result, neg, zero, overflow);
9
10     initial
11     begin
12         $monitor("ALUOp: %d, Input A: %d, Input B: %d, Result: %d,
13                 Negative: %d, Zero: %d, Overflow: %d", ALUOp, a,
14                 b, result, neg, zero, overflow);
15         ALUOp = 4'b0001; a = 0; b = 0;
16         #10; a = 43; b = 25;
17         #10; ALUOp = 4'b0010;
```

```
18     #10; ALUOp = 4'b0011;
19     #10; ALUOp = 4'b0100;
20     #10; ALUOp = 4'b0101;
21     #10; a = 16'b0111111111111111; b = 16'b0111111111111111;
22     ALUOp = 4'b0001;
23     #10; a = 16'b0111111111111111; b = 16'b1111111111111111;
24     ALUOp = 4'b0101;
25     #10; a = 200; b = 200; ALUOp = 4'b0101;
26     #10; a = 60; b = 2; ALUOp = 4'b0110;
27     #10; ALUOp = 4'b0111;
28     #10; ALUOp = 4'b1000;
29     #10; ALUOp = 4'b1001;
30     #10; a = -60; b = 2; ALUOp = 4'b0110;
31     #10; ALUOp = 4'b0111;
32     #10; ALUOp = 4'b1000;
33     #10; ALUOp = 4'b1001;
34     #10; ALUOp = 4'b0000;
35     end
36 endmodule
```

B.3 Sign Extender

```
1 module sign_ext_tb();
2     reg [1:0] SignOp;
3     reg [9:0] In0;
4     reg [3:0] In1;
5     reg [5:0] In2;
6     reg [7:0] In3;
7     wire [15:0] ExOut;
8
9     sign_ext SE (SignOp, In0, In1, In2, In3, ExOut);
10
11     initial
12     begin
13         $monitor("SignOp: %d, In0: %d, In1: %d, In2: %d, In3: %d,
14                 ExOut: %d", SignOp, In0, In1, In2, In3, ExOut);
15         In0 = 10'b0010111010; In1 = 4'b0110; In2 = 6'b001101;
16         In3 = 8'b00100101; SignOp = 0;
17         #10; SignOp = 1;
18         #10; SignOp = 2;
19         #10; SignOp = 3;
```

```
20         #10; In0 = 10'b1010111010; In1 = 4'b1110; In2 = 6'b101101;
21         In3 = 8'b10100101; SignOp = 0;
22         #10; SignOp = 1;
23         #10; SignOp = 2;
24         #10; SignOp = 3;
25     end
26 endmodule
```

B.4 Move Extender

```
1 module mov_ext_tb();
2     reg MovOp;
3     reg [7:0] MovIn;
4     wire [15:0] MovOut;
5
6     mov_ext ME (MovOp, MovIn, MovOut);
7
8     initial
9     begin
10        $monitor("MovOp: %d, MovIn: %d, MovOut: %d", MovOp, MovIn, MovOut);
11        MovIn = 8'b11111111; MovOp = 0;
12        #10; MovOp = 1;
13        #10; MovIn = 1; MovOp = 0;
14        #10; MovOp = 1;
15    end
16 endmodule
```

B.5 Adder

```
1 module adder_tb();
2     reg [15:0] a;
3     reg [15:0] b;
4     wire [15:0] result;
5
6     adder ADD (a, b, result);
7
8     initial
9     begin
10        $monitor("Input A: %d, Input B: %d, Result: %d", a, b, result);
11        a = 0; b = 0;
```

```
12         #10; a = 10; b = 20;
13         #10; a = 13000; b = 20000;
14         #10; a = 16000; b = 8000;
15         #10; a = 42000; b = 69;
16     end
17 endmodule
```

B.6 Control Unit

```
1 module control_tb();
2     reg [3:0] op;
3     reg r;
4     reg [1:0] ls, ad;
5     wire [1:0] SignOp, MuxC0, MuxC1, MuxC2, MuxC3, MuxC4;
6     wire MovOp, RegW, MemW, MemR;
7     wire [2:0] BrOp;
8     wire [3:0] ALUOp;
9
10    control CON (op, r, ls, ad, RegW, MemR, MemW, BrOp, ALUOp, MovOp,
11                SignOp, MuxC0, MuxC1, MuxC2, MuxC3, MuxC4);
12
13    initial
14    begin
15        $monitor("Opcode: %d, R Field: %d, LS Field: %d, AD Field: %d,
16                RegW: %d, MemR: %d, MemW: %d, BrOp: %d, ALUOp: %d,
17                MovOp: %d, SignOp: %d, MuxC0: %d, MuxC1: %d, MuxC2: %d,
18                MuxC3: %d, MuxC4: %d", op, r, ls, ad, RegW, MemR, MemW,
19                BrOp, ALUOp, MovOp, SignOp, MuxC0, MuxC1, MuxC2, MuxC3,
20                MuxC4);
21        op = 4'b0001; r = 0; ls = 0; ad = 0;
22        #10; op = 4'b0010;
23        #10; op = 4'b0011;
24        #10; op = 4'b0100;
25        #10; op = 4'b0101;
26        #10; op = 4'b0110;
27        #10; op = 4'b0111;
28        #10; op = 4'b1000;
29        #10; op = 4'b1001;
30        #10; r = 1; op = 4'b1001;
31        #10; op = 4'b1010;
32        #10; op = 4'b1011;
```

```
33         #10; op = 4'b1100;
34         #10; op = 4'b1101;
35         #10; ls = 2'b10; op = 4'b1110;
36         #10; ls = 2'b01; op = 4'b1110;
37         #10; op = 4'b1111;
38         #10; ad = 2'b10; op = 4'b1111;
39         #10; ad = 2'b01; op = 4'b1111;
40         #10; ad = 2'b11; op = 4'b1111;
41         #10; op = 4'b0000;
42     end
43 endmodule
```

B.7 Branch Control Unit

```
1 module branch_control_tb();
2     reg [2:0] BrOp;
3     reg neg;
4     reg zero;
5     wire [1:0] muxc5;
6
7     branch_control BRC (BrOp, neg, zero, muxc5);
8
9     initial
10    begin
11        $monitor("BrOp: %d, Negative: %d, Zero: %d, MuxC5(output): %d",
12                BrOp, neg, zero, muxc5);
13        neg = 0; zero = 0; BrOp = 3'b000;
14        #10; BrOp = 3'b001;
15        #10; BrOp = 3'b110;
16        #10; BrOp = 3'b010;
17        #10; zero = 1; BrOp = 3'b010;
18        #10; BrOp = 3'b011;
19        #10; zero = 0; BrOp = 3'b011;
20        #10; BrOp = 3'b100;
21        #10; neg = 1; BrOp = 3'b100;
22        #10; BrOp = 3'b101;
23        #10; neg = 0; BrOp = 3'b101;
24    end
25 endmodule
```

B.8 4-to-1 Multiplexer

```
1 module mux_4to1_tb();
2     reg [1:0] control;
3     reg [15:0] a;
4     reg [15:0] b;
5     reg [15:0] c;
6     reg [15:0] d;
7     wire [15:0] out;
8
9     mux_4to1 M1 (control, a, b, c, d, out);
10
11     initial
12     begin
13         $monitor("Control: %d, Input A: %d, Input B: %d, Input C: %d,
14                 Input D: %d, Output: %d", control, a, b, c, d, out);
15         a = 1; b = 2; c = 3; d = 4; control = 0;
16         #10; control = 1;
17         #10; control = 2;
18         #10; control = 3;
19     end
20 endmodule
```

B.9 Program Counter

```
1 module pc_tb();
2     reg clk;
3     reg [9:0] in;
4     wire [9:0] out;
5
6     pc PC1 (clk, in, out);
7
8     initial
9     begin
10         $monitor("Clock: %d, In: %d, Out: %d", clk, in, out);
11         in = 10'b1010101010; clk = 0;
12         #10; in = 10'b1111111111;
13         #10; in = 0;
14     end
15
16     always
```



```
17     begin
18         #5; clk = ~clk;
19     end
20 endmodule
```